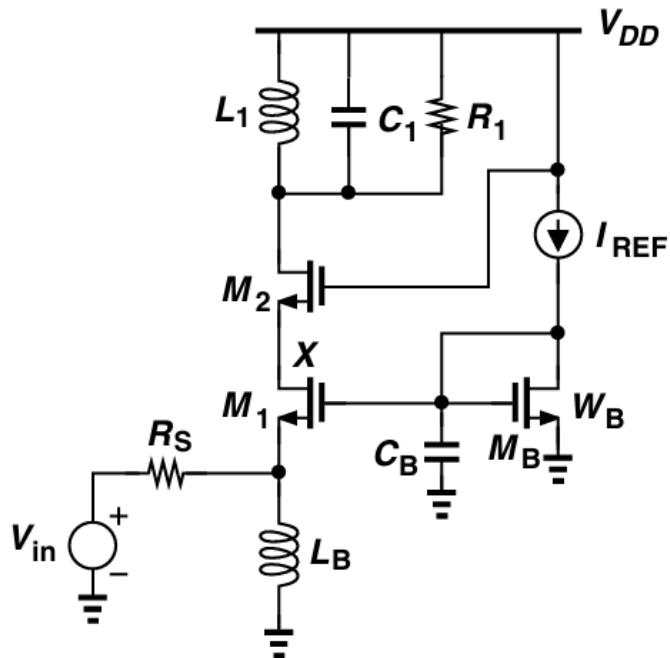


Name: Thong Thach

# LNA DESIGN PROJECT


Based on this schematic of the biasing cascode CG stage LNA from the textbook



**Figure 5.24** Biasing of cascode CG stage.

Design all the parameters will be followed below:

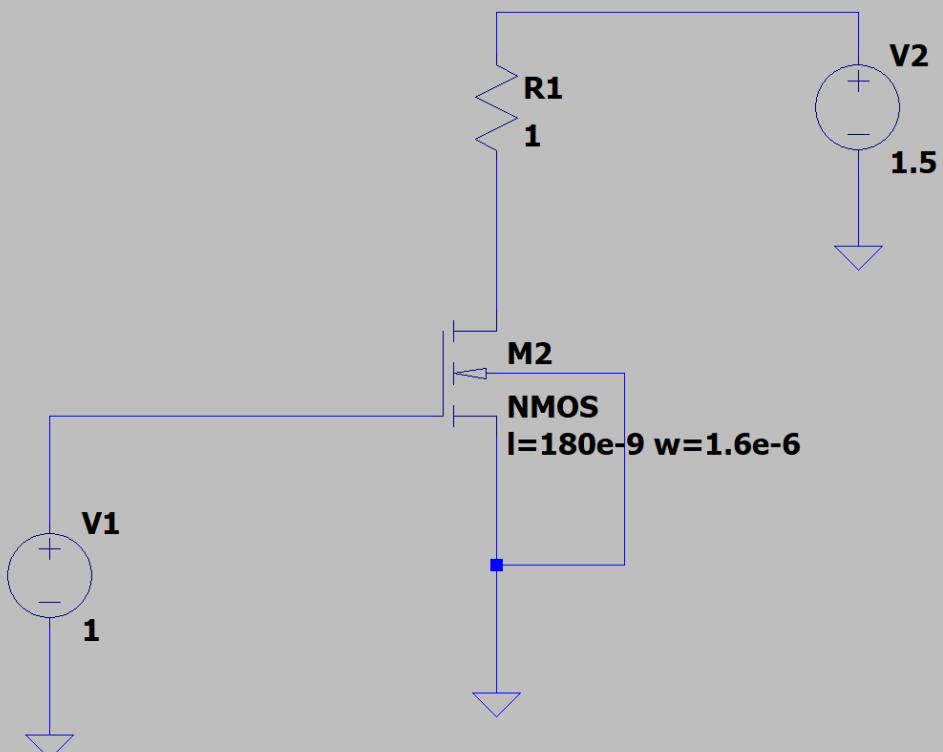**Step 1: Sizing and biasing of cascode M1**





**.dc V1 0 1.5 0.01**

**.include "C:\Users\thong\Downloads\myspicemodels.txt"**

**.op**

Plot between Id(M2) and the gm

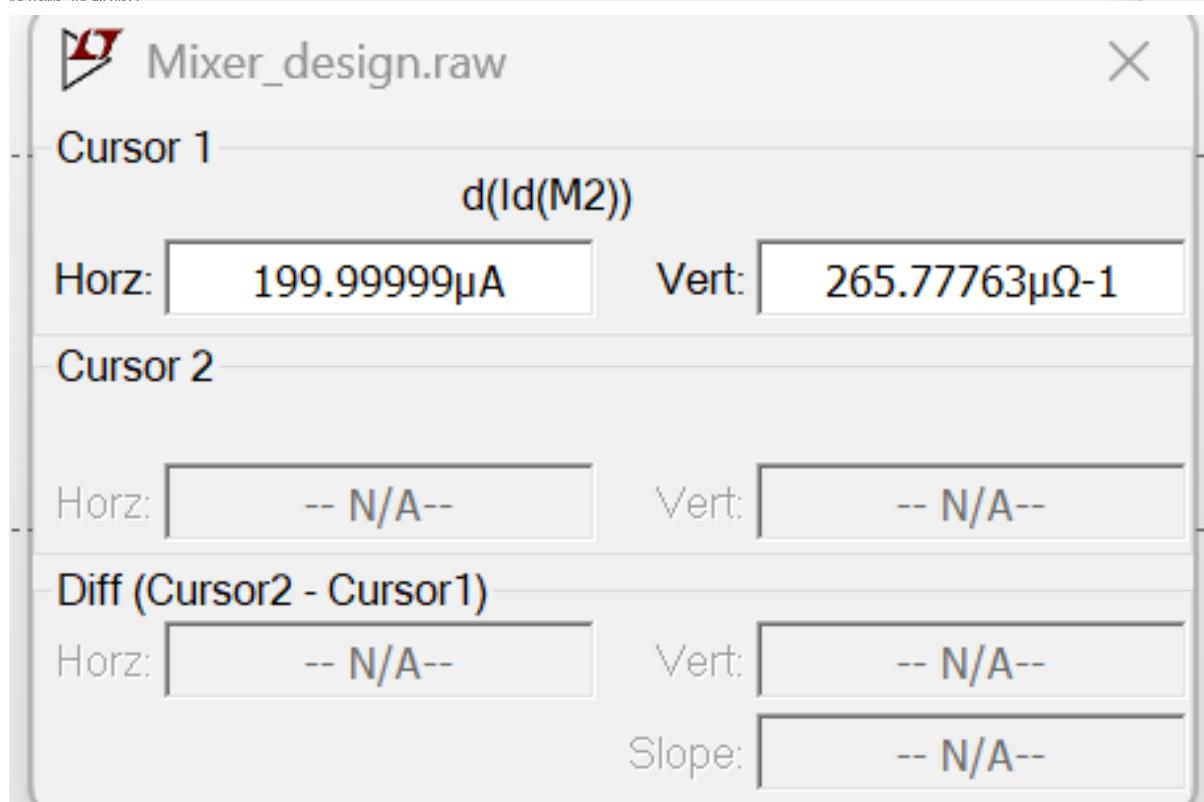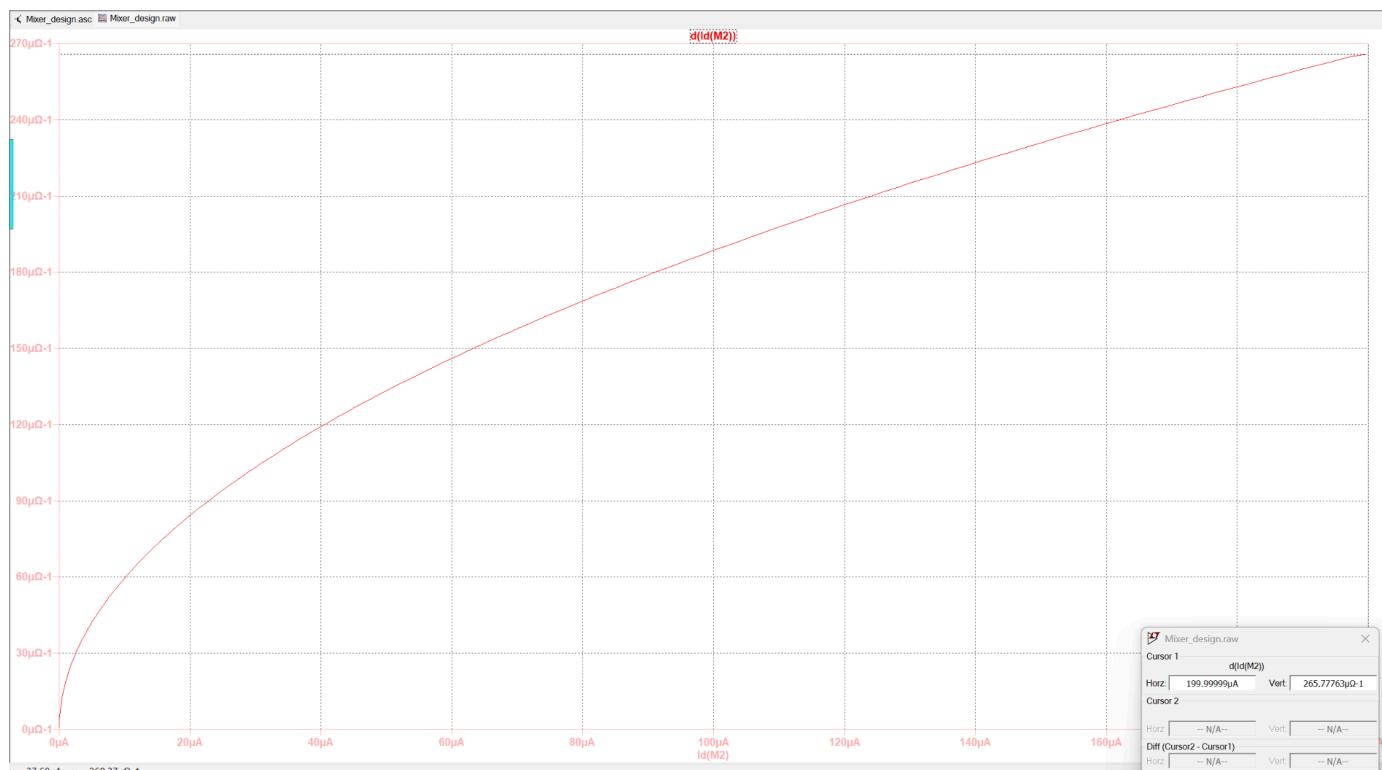



Mixer\_design.raw



### Cursor 1

$d(Id(M2))$

Horz:  Vert:

### Cursor 2

Horz:  Vert:

### Diff (Cursor2 - Cursor1)

Horz:  Vert:

Slope:

$$g_{m, \max} = 265.78 \mu S$$

①

$$\Rightarrow 80\% g_{m, \max} = \frac{265.78 (80)}{100} = 212.6 \Rightarrow I_{d0} = 126.6 \mu A$$

$$\text{Scaling factor } \alpha = \frac{g_{m1}}{g_{m0}} = \frac{0.025}{212.6 \mu S} = 94$$

$$\Rightarrow W_1 = 94 \quad W_0 = 94 (1.6) = 150.4 \mu m.$$

$$I_d = 94 I_{d0} = 94 (126.6 \mu A) = 11900.4 \\ = 1.2 mA$$

$$C_{total} = C_{pad} + C_{SB1} + C_{GS1} \quad \text{(Calculating } L_B \text{ and } R_B)$$

$$\text{Since } C_{GS1} = \frac{2}{3} W_1 L_1 C_{ox} + W_1 C_{ov}$$

$$\Rightarrow C_{GS1} = \frac{2}{3} (150.4 \mu m) (180 \cdot 10^{-9}) (0.508) + (150.4 \mu m) (2.8 \cdot 10^{-10})$$

$$\Rightarrow C_{GS1} = 91.6 fF^{12} + 42 fF^{-14}$$

$$\Rightarrow C_{GS1} = 133.6 fF^{12}$$

$$C_{SB_1} = w_1 E C_j + 2(w_1 + E) C_{jsw} \quad (2)$$

$$\Rightarrow C_{SB_1} = 150.4 \mu m (1 \mu m) (3.82 \cdot 10^{-4}) + 2(150.4 \mu m + 1 \mu m) (0.78 \cdot 10^{-10})$$

$$\Rightarrow C_{SB_1} = 575 \cdot 10^{-16} + 236 \cdot 10^{-16}$$

$$\Rightarrow C_{SB_1} = 811 \cdot 10^{-16}$$

$$\Rightarrow C_{SB_1} = -81.18 F$$

$$\Rightarrow C_{total} = C_{GS_1} + C_{SB_1} + C_{pad}$$

$$\Rightarrow C_{total} = 133.68 F + 81.18 F + 50 F$$

$$\Rightarrow C_{total} = 264.78 F$$

$$u = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{u^2 C}$$

$$\Rightarrow L = \frac{1}{(2\pi(2.4 \cdot 10^9))^2 (264.78 F)}$$

$$\Rightarrow L_B = 16.6 \text{ nH}$$

$$R_B = Q L_B u$$

$$\Rightarrow R_B = 10 (16.6 \cdot 10^{-9}) (2\pi(2.4 \cdot 10^9))$$

$$\Rightarrow R_B = 2503 \text{ ohms.}$$

Calculating  $M_1$  and  $M_B$ .

(3)

$$w_B = 0.2 w_1$$

$$\Rightarrow w_B = 0.2(150.4 \mu m) = [30.08 \mu m]$$

$$\Rightarrow I_{ref} = 0.2 I_{d1} = 0.2(1.2 \text{ mA}) = [0.24 \text{ mA}]$$

The width of  $M_1 = M_2 = [150.4 \mu m]$

Finding  $L_1$  and  $R_1$

$$\Rightarrow C_{out} = C_1 = C_{load} + C_{GD_2} + C_{DB_2}$$

$$\Rightarrow C_1 = 40 \text{ fF} + W_c C_{ox} + C_{SB_1}$$

$$\Rightarrow C_1 = 40 \text{ fF} + 42 \text{ fF} + 91.6 \text{ fF}$$

$$\Rightarrow [C_1 = 173.6 \text{ fF}]$$

$$\Rightarrow L_1 = \frac{1}{w^2 c}$$

$$\Rightarrow L_1 = \frac{1}{(2\pi(2.4 \cdot 10^9))^2 (173.6 \text{ fF})}$$


$$\Rightarrow [L_1 = 25.4 \text{ nH}]$$

$$\Rightarrow R_1 = \rho L_1 w$$



$$\Rightarrow R_1 = 10(25.4 \cdot 10^{-9})(2\pi(2.4 \cdot 10^9))$$

$$\Rightarrow [R_1 = 3830 \text{ ohms.}]$$
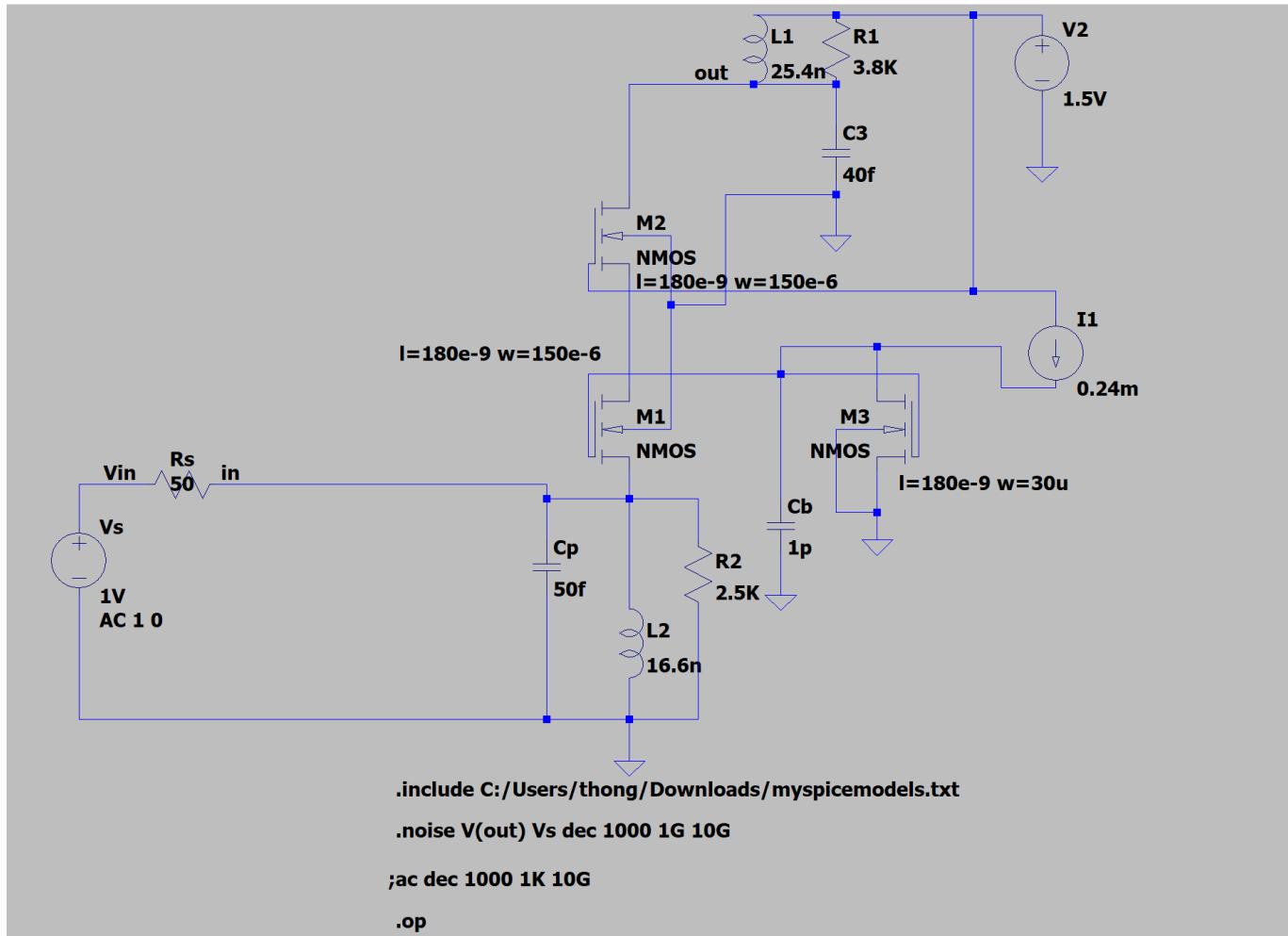
### CG STAGE LNA DESIGN without ro effect:



NF from the simulation:

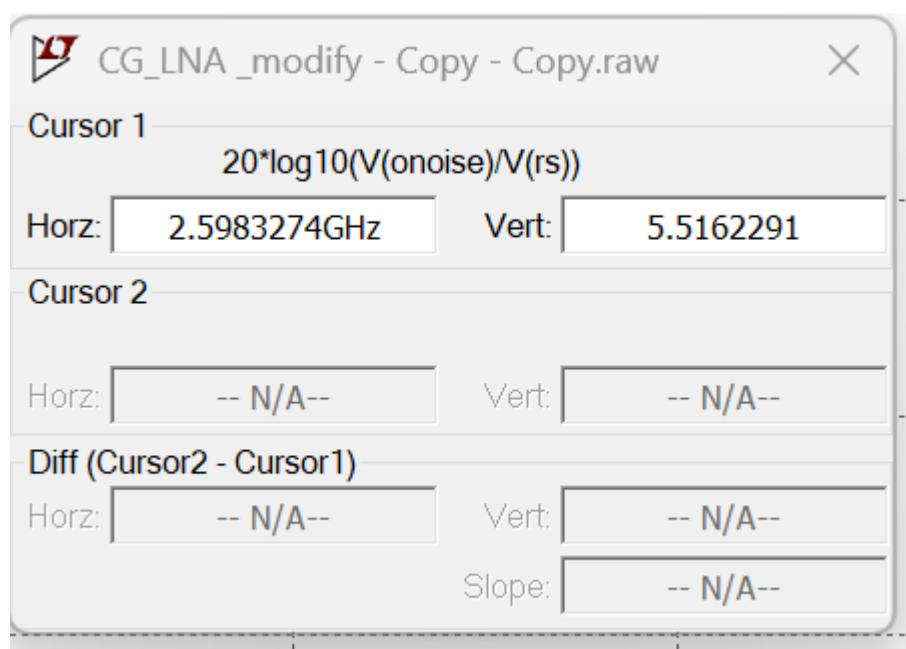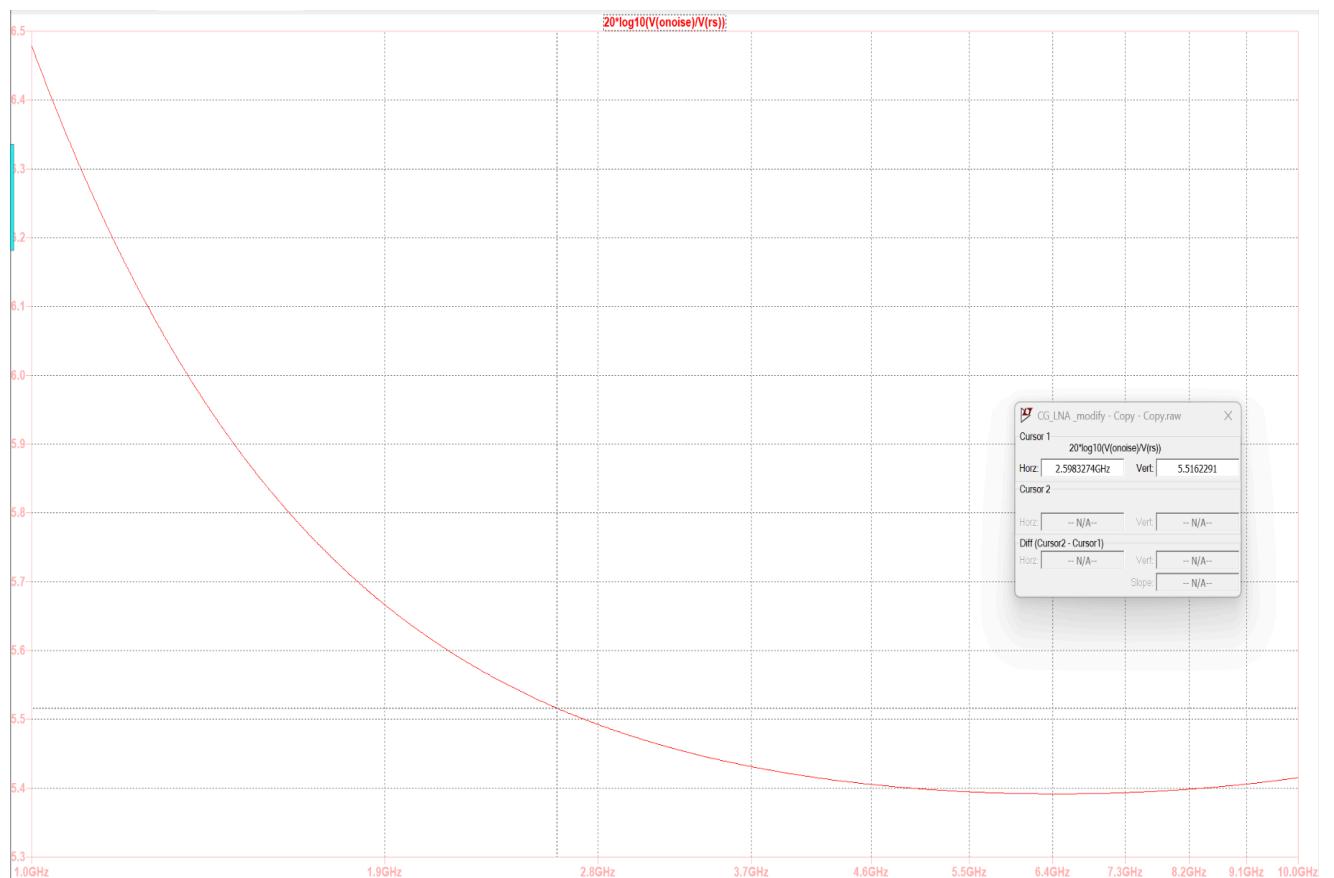

**NF = 5.5**

**NF calculation from the theory:**

without  $r_o$  channel length.

①

$$NF_{M_1} = \frac{4kT\psi(gm_1 A_V^2)}{4kTR_s A_V^2} = \boxed{\psi}$$

$NF_{M_2} = \frac{4kT\psi(gm_2 A_V^2)}{4kTR_s A_V^2}$  but since  $r_o$  is large  $\Rightarrow M_2$  is negligible.

$$NF_{R_1} = \frac{4kTR_1}{4kTR_s(A_V)^2} = \boxed{\frac{R_1}{R_s(A_V)^2}}$$

$$NF_{R_B} = \frac{4kTR_B (A_V)^2 \cdot (r_s/2R_B)^2}{4kTR_s (A_V)^2}$$

$$= \boxed{\frac{R_B}{R_s} \left( \frac{r_s}{2R_B} \right)^2}$$

Gain (based on textbook p. 282) ( $\frac{v_{out}}{v_{in}} = \frac{R_1}{2R_s}$ )

$$\Rightarrow \frac{R_1}{2R_s} = \frac{6.3 \cdot 10^3}{2(50)} = 63 \text{ E gain is too large.}$$

$$\Rightarrow NF_{M_1} = \boxed{\psi}$$

$$NF_{R_1} = \frac{R_1}{R_s \left( \frac{R_1}{2R_s} \right)^2} = \frac{R_1}{R_s \left( \frac{R_1^2}{4R_s^2} \right)} = \frac{R_1}{\frac{R_s R_1^2}{4R_s^2}} = \frac{1}{\frac{R_1}{4R_s}}$$

$$= \boxed{\frac{4R_s}{R_1}}$$

$$NF_{R_B} = \frac{R_B}{R_s} \frac{R_s^2}{4R_B^2}$$

$$\Rightarrow NF_{R_B} = \boxed{\frac{R_s}{4R_B}}$$

$$\Rightarrow NF_{total} = 1 + \psi + \frac{4R_s}{R_1} + \frac{R_s}{4R_B}$$

$$NF_{total} = 1 + \frac{2}{3} + \frac{4(50)}{3.8 \cdot 10^3} + \frac{50}{4(2.5 \cdot 10^3)} \quad (2)$$

$$\Rightarrow NF_{total} = 1.72 \approx \boxed{2.4 \text{ dB}}$$


**NF = 2.4**


Since the NF from the simulation is too high ( 5.5 and 2.4), the difference is **3.1 dB**.

- > considered adding the L-matching network will reduce the noise figure of the LNA circuit
- > LNA CG stage design with the  $r_o$  effect

#### **CG STAGE LNA DESIGN with $r_o$ effect:**

**Finding  $r_o$ :**

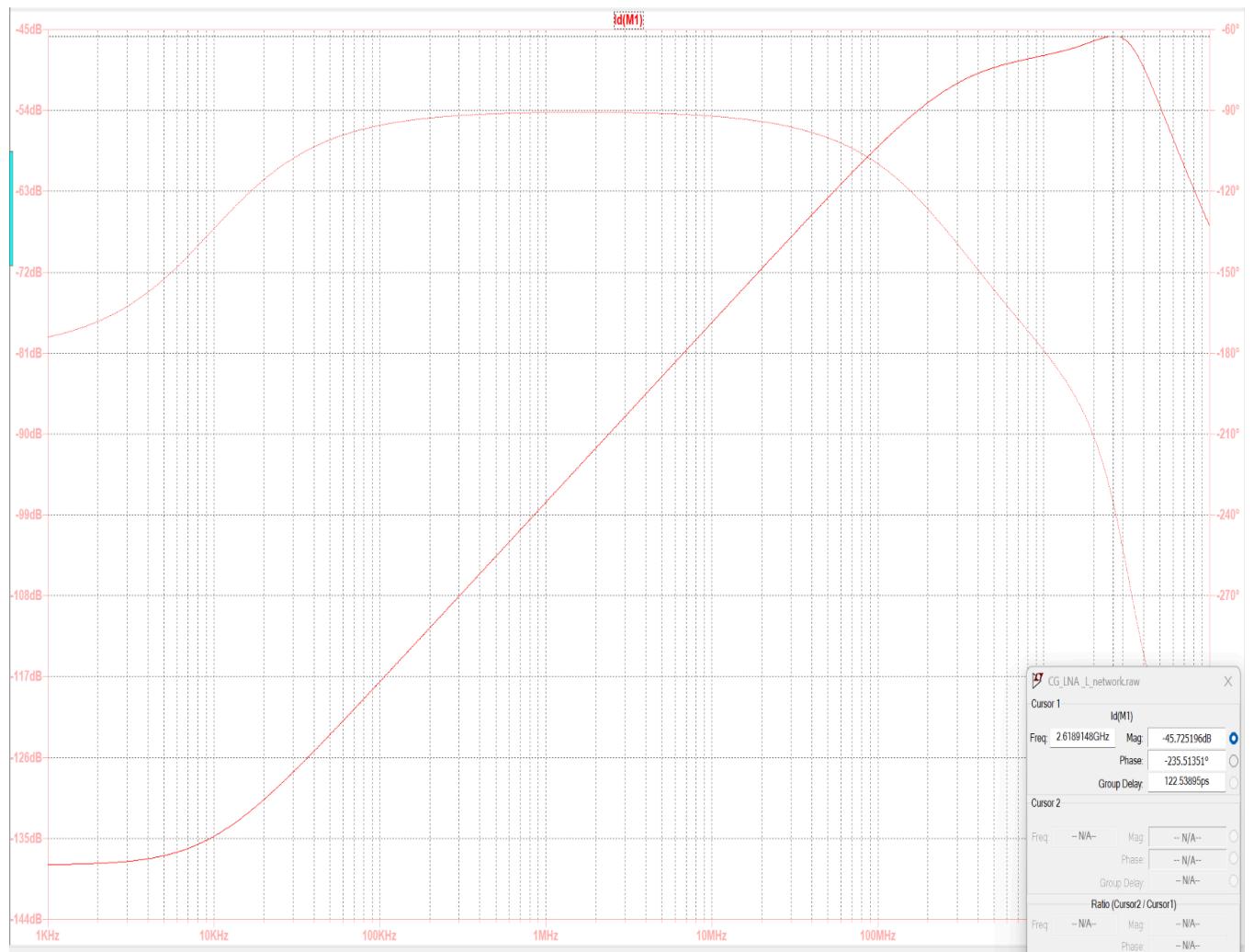


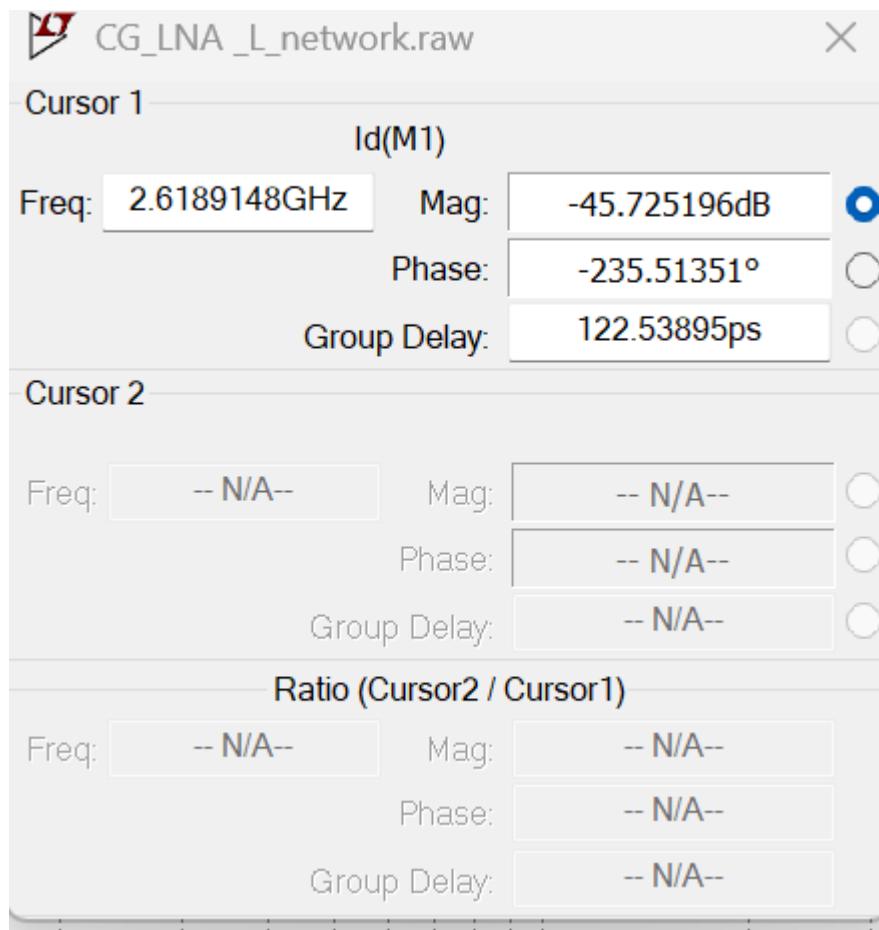


$$-45.8 = 20 \cdot \log(\text{Id})$$

$$\rightarrow \text{Id} = 10^{(-45.8/20)} = 5.1 \cdot 10^{-3}$$

**Finding the gain of the LNA from the simulation:**

**NF from the simulation:**

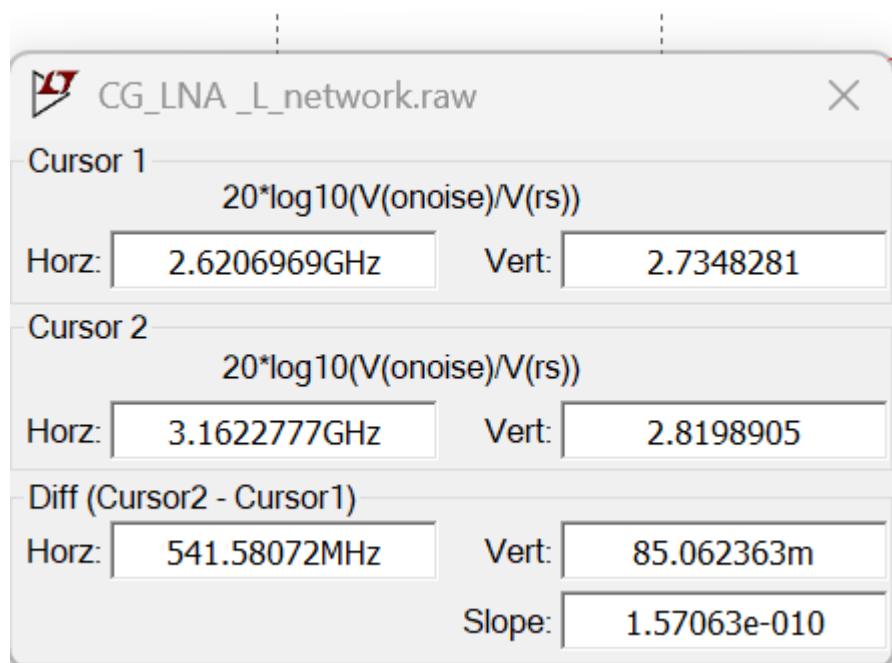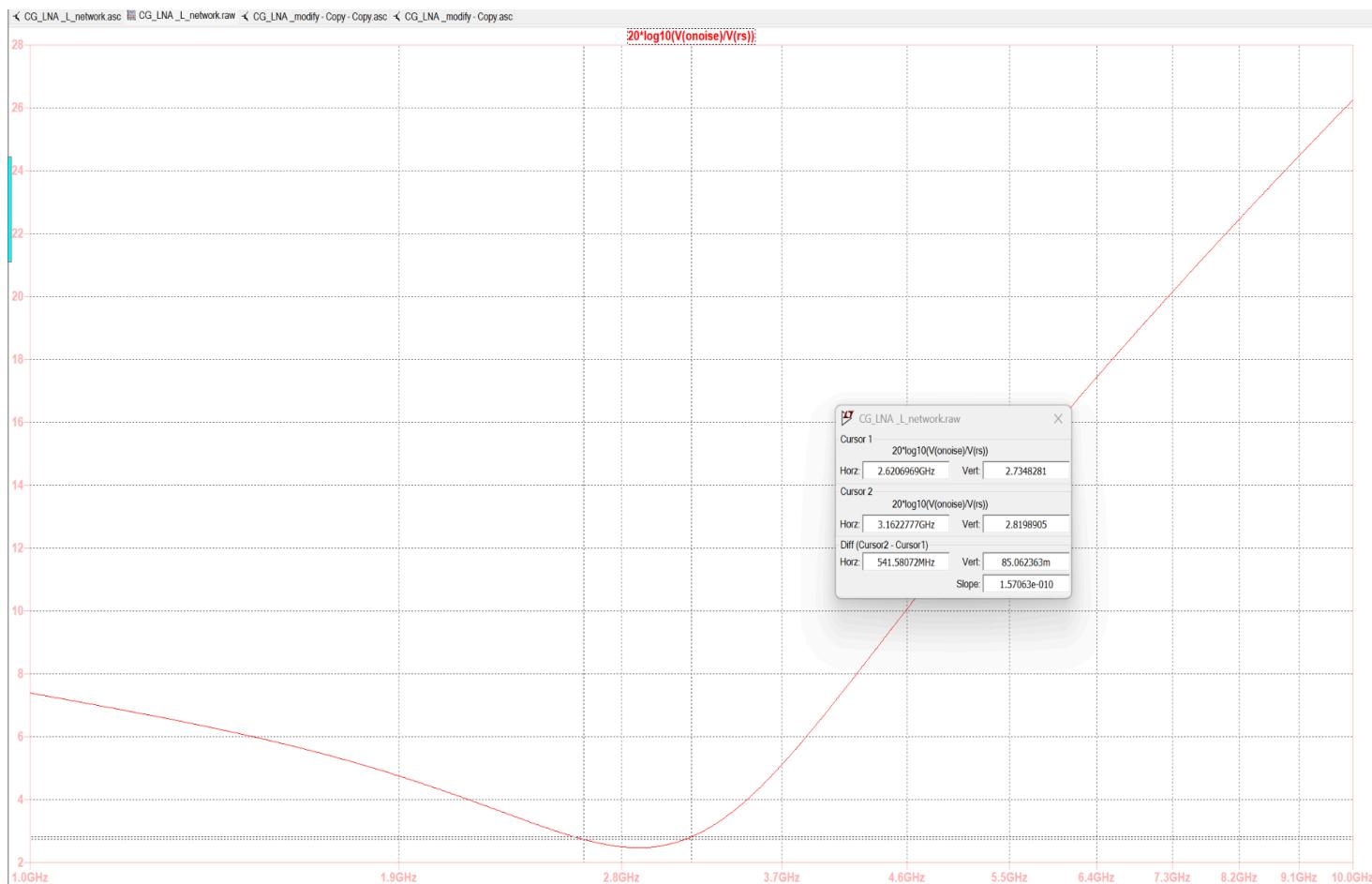

**NF = 2.73**


**NF from the theory:**

## Noise Figure

①

NF

For the NF of M1:

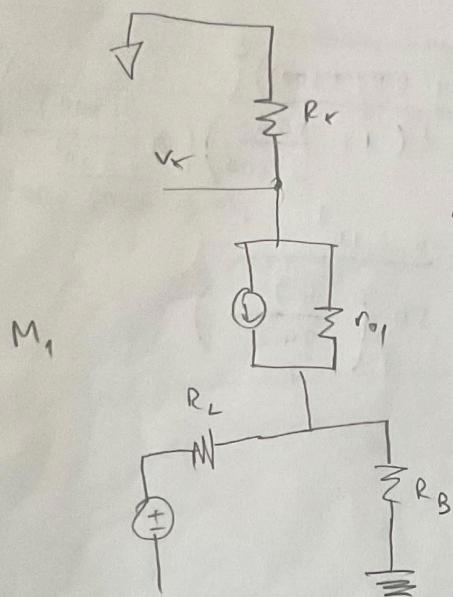

$$\text{Thermal noise output } (4K\bar{T}\Phi/gm_1)A_V^2$$

$$\Rightarrow \frac{4K\bar{T}\Phi/gm_1}{2} \left( \frac{A_V^2}{2} \right)$$


$$\langle v_{n,out,M1} \rangle^2 = \frac{4K\bar{T}\Phi/gm_1}{4K\bar{T}R_S A_V^2} \quad R_S = \frac{1}{gm}$$

$$\Rightarrow \frac{\Phi/gm}{4R_S} = \frac{\Phi}{4R_S gm} = \boxed{\frac{\Phi}{4}}$$

Since  $R_B \gg R_L \rightarrow G_m = G_m(R_{in}/2R_B)$

$$\Rightarrow \langle v_{n,out,R_B} \rangle^2 = \frac{4K\bar{T}R_B (G_m \frac{R_{in}}{2R_B})^2}{4K\bar{T}R_S G_m^2}$$
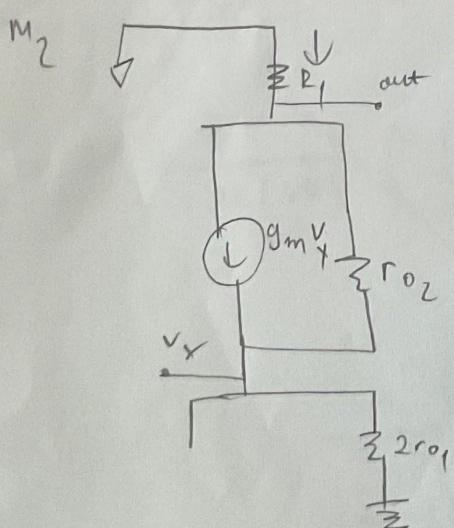
$$= \frac{R_B R_{in}^2}{4R_S R_B^2} = \boxed{\frac{R_{in}^2}{4R_S R_B}}$$



$$\langle v_{n,out,r_o2} \rangle^2 = \boxed{4K\bar{T}\Phi/gm_2 A_V^2}$$

Since  $v_x = 2.6 \text{ GHz} > 2.4 \text{ GHz}$

Source degeneration CS stage.

$$\Rightarrow V_{out} = V_{in} + I_2 r_{o2}$$

$$I_{out} = g_m v_{AS} + I_2$$

$$\Rightarrow I_2 = g_m v_{AS} - I_{out}$$

$$\Rightarrow V_{out} = V_{in} + (g_m v_{AS}) r_{o2}$$

$$\Rightarrow V_{out} = (V_{in} - V_{AS}) + (g_m v_{AS}) r_{o2}$$

$$\Rightarrow V_{\text{out}} = V_{\text{in}} - V_{\text{diss}} + g_m V_{\text{diss}} r_{o2} \quad (2)$$

$$\Rightarrow V_{\text{out}} = V_{\text{in}} - V_{\text{diss}} (1 + g_m r_{o2}).$$

$$\Rightarrow \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{g_m r_{o2} R_1}{R_1 + 2r_{o1} + r_{o2} + g_m r_{o2} 2r_{o1}} = A_V$$

$\rightarrow$  NF of  $M_2$ :

$$\Rightarrow \frac{4KT \gamma / g_m^2}{4KT R_S \left( \frac{(1 + g_m r_{o2})(1 + g_m r_{o1})}{\left(1 + \frac{r_{o2}}{R_{\text{out}}}\right) \left(2 + \frac{2r_{o1}}{R_X}\right)} \right)^2}$$

$$\Rightarrow \frac{4}{g_m R_S} \left( \frac{A_V}{G_m} \right)^2. \quad R_X = \frac{R_1 + r_{o2}}{1 + g_m r_{o2}} \approx \frac{R_1}{g_m r_{o2}}$$

$$\Rightarrow \frac{\frac{2}{3}}{0.02(50)} \left( \frac{(1 + 0.02 \cdot (300))(1 + 0.02 \cdot 300)}{\left(1 + \frac{300}{2(300)}\right) \left(2 + \frac{2(300)}{6 \cdot 10^3}\right)} \right)^2$$

$$= \frac{2}{3} \left( \frac{\frac{49}{3}}{\frac{3}{2} \left(2 + \frac{2 \cdot 300}{1050}\right)} \right) = \frac{2}{3} \left( \frac{\frac{49}{3}}{\frac{3}{2} \left(\frac{18}{7}\right)} \right) = \frac{2}{3} \left( \frac{49}{27} \right)^2 = 107.59.$$

$$NF_{R_1} = \frac{4KTR_1}{4KTR_S(G_m)^2} = \frac{R_1}{R_S(G_m)^2} \quad (3)$$

$$= \frac{3.8 \cdot 10^3}{50 (15.1)^2}$$

$$= \boxed{0.33}$$

$$NF_{M_1} = \frac{4}{4} = \frac{\frac{2}{3}}{\frac{4}{4}} = \boxed{\frac{1}{6}}$$

$$NF_{R_B} = \frac{163.9^2}{4(50)(2.5 \cdot 10^3)}$$

$$\Rightarrow NF_{R_B} = \boxed{0.054}$$

$$R_{in} = \frac{1}{g_{m_1}} + \frac{R_1}{g_{m_1} r_o g_{m_2} r_o} + \frac{1}{g_{m_2} r_o g_{m_2}}$$

$$\Rightarrow R_{in} = \frac{1}{0.02} + \frac{3.8 \cdot 10^3}{0.02(300)(0.02)(300)} + \frac{1}{0.02(300)(0.02)}$$

$$\Rightarrow R_{in} = 50 + 10556 + 8.33.$$

$$\Rightarrow R_{in} = 163.9.$$

$$NF_{M_2} = \frac{4}{g_{m_2} R_S} \left( \frac{A_v}{g_{m_2}} \right)^2$$

$$A_v = \frac{g_{m_2} r_o R_1}{R_1 + 2r_o + r_o + g_{m_2} r_o^2 r_o}$$

$$\Rightarrow A_v = \frac{0.02 (300) (3.8 \cdot 10^3)}{3.8 \cdot 10^3 + 2(300) + 300 + 0.05(300)2(300)}$$

$$\Rightarrow A_v = \frac{22800}{13700} = \boxed{1.66}$$

$$\Rightarrow NF_{M_2} = \frac{\frac{2}{3}}{0.02(50)} \left( \frac{1.66}{15.1} \right)^2 \quad (4)$$

$$\Rightarrow NF_{M_2} = \frac{2}{3} \cdot 0.012$$

$$\Rightarrow NF_{M_2} = 8 \cdot 10^{-3}$$

$$NF_{total} = 1 + NF_M_1 + NF_{M_2} + NF_{R_B} + NF_{R_I}$$

$$= 1 + \frac{1}{6} + 8 \cdot 10^{-3} + 0.054 + 0.33$$

$$= 1.56$$

**NF = 1.56**


→ The difference between the NF from the simulation and the theory:

$$2.73 - 1.56 = 1.17 \text{ dB}$$

As the observation between the NF of CG Cascode LNA with ro effect and without ro effect, the ro effect will reduce the noise figure significantly compares to CG Cascode LNA without ro effect.


#### Altium design for LNA CG Stage


For the schematic design:

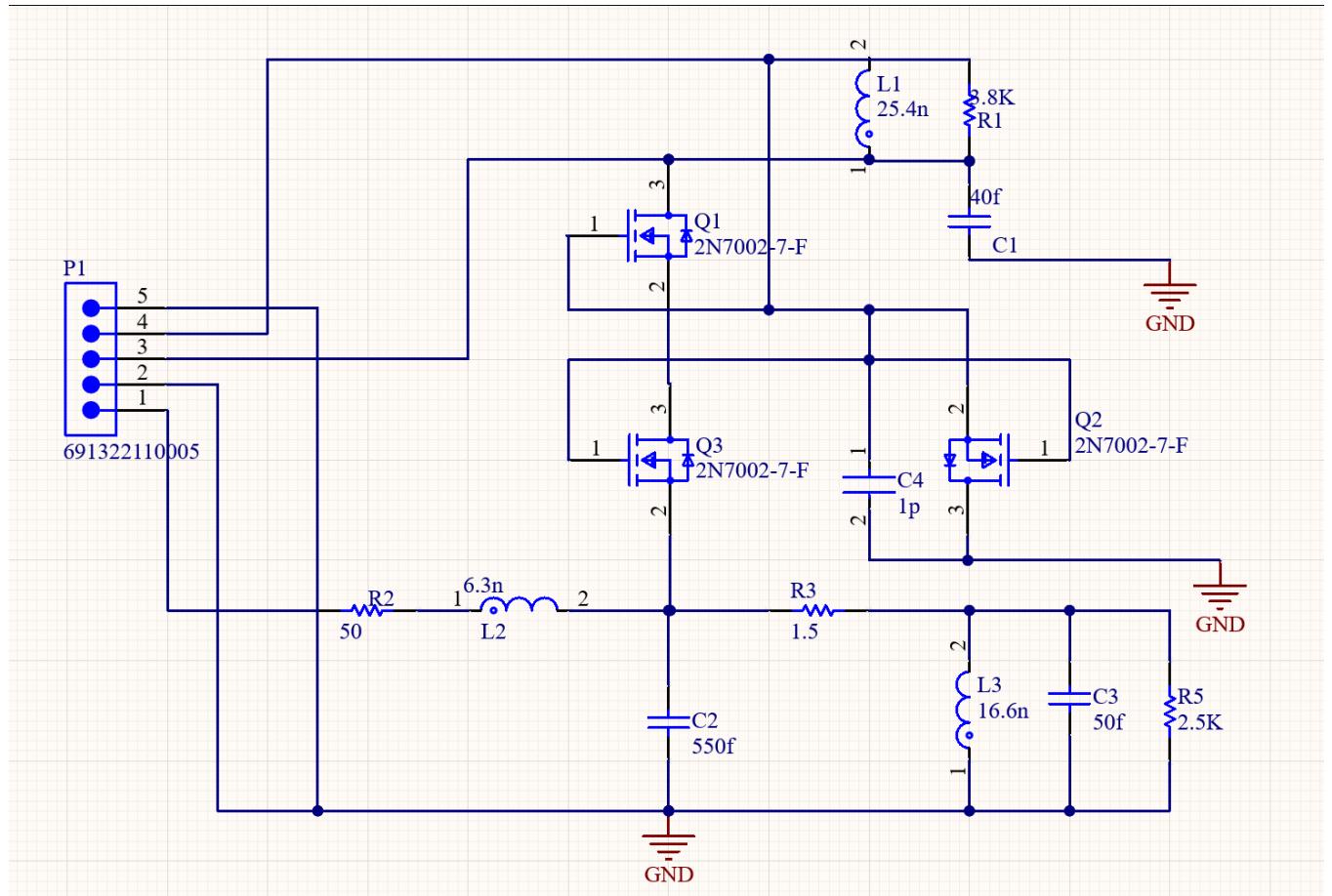

**For the PCB Design:**

P1

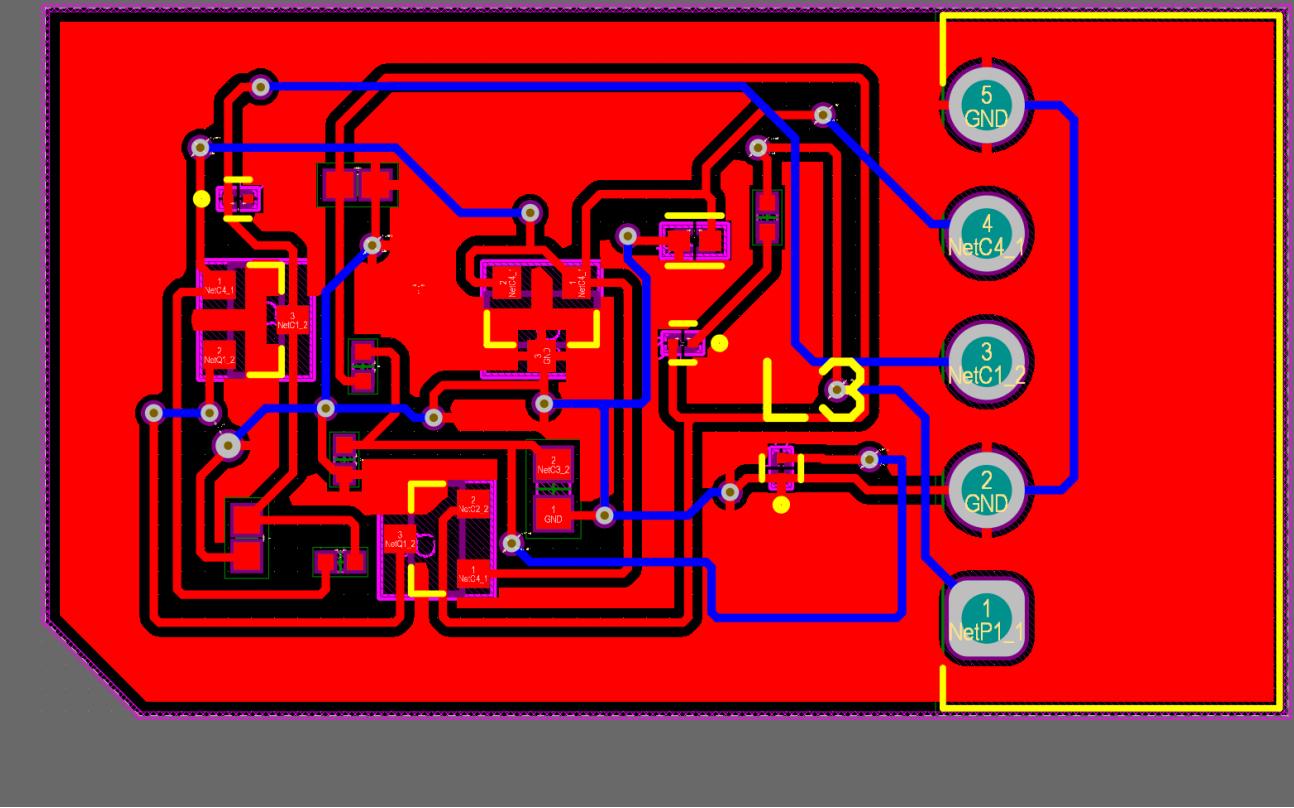

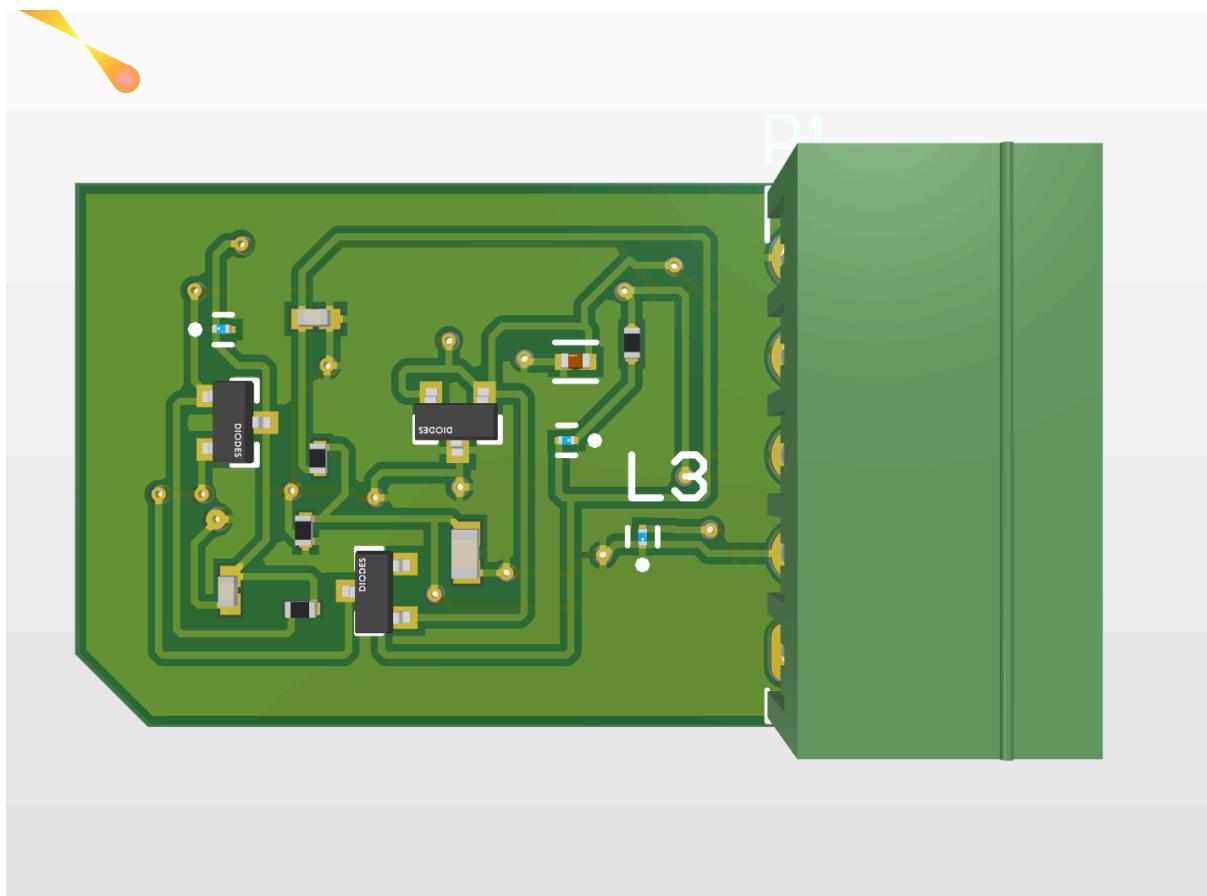


## HANDS-DRAWING LAYOUT:

### FOR THE WIDTH AND LENGTH:

Based on RF Microelectric textbook reference from Behzad Razavi

$W_1 = W_2$ , such a structure can be expanded to one with multiple gate fingers.

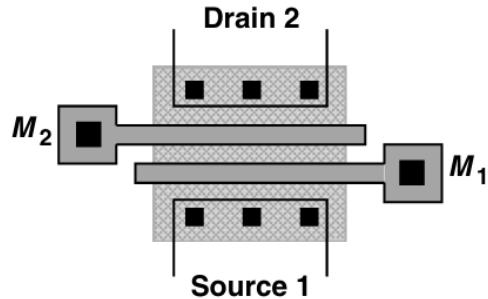


**Figure 5.27** Layout of cascode devices.


**L= 180e-9**

**W= 81e-6**

### FOR THE INDUCTOR:

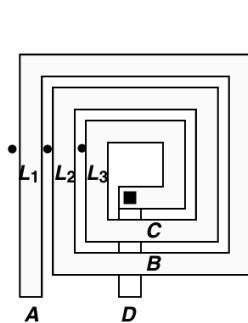

**Figure 7.4** Simple spiral inductor.

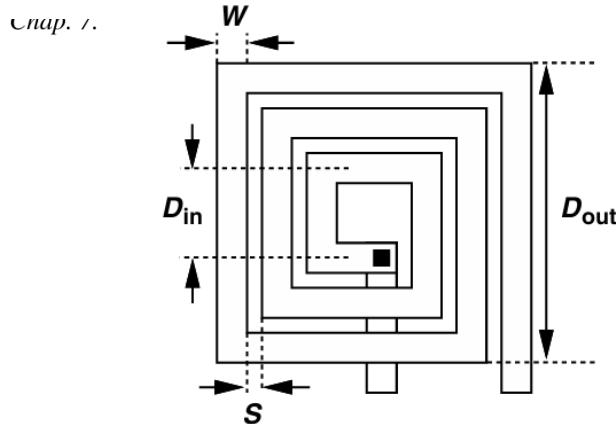

$$l_{tot} \approx 4N[D_{out} - W - (N - 1)(W + S)]. \quad (7.12)$$

$$L \approx 1.3 \times 10^{-7} \frac{l_{tot}^{5/3}}{\left[ \frac{l_{tot}}{4N} + W + (N - 1)(W + S) \right]^{1/3}} W^{0.083} (W + S)^{0.25}. \quad (7.15)$$

For the optimal width of  $M_2$ :

$\Rightarrow L$  and  $w$  of  $M_2$  equals to  $L$  and  $w$  of  $M_1$ .

For the inductor design:  $D_{\text{air}} \approx 200 \mu\text{m}$  as the pitch with  
 $N = 3$ ,  $w = 4 \mu\text{m}$ , and  $s = 0.5 \mu\text{m}$ ,

$$l_{\text{total}} = 4N [D_{\text{air}} - w - (N-1)(w+s)]$$

$$= 4(3) [200 \mu\text{m} - 4 \mu\text{m} - (3-1)(4 \mu\text{m} + 0.5 \mu\text{m})]$$

$$= 2244 \mu\text{m}$$

$$\Rightarrow L = 1.3 \cdot 10^{-7} \frac{l_{\text{total}}}{(2244 \mu\text{m})^{5/3}}$$

$$\left( \frac{l_{\text{total}}}{4N} + w + (N-1)(w+s) \right) w^{0.083} (w+s)^{0.25}$$

$$\Rightarrow L = 1.3 \cdot 10^{-7} \frac{(2244 \mu\text{m})^{5/3}}{\left( \frac{2244 \mu\text{m}}{4(3)} + 4 \mu\text{m} + (3-1)(4 \mu\text{m} + 0.5 \mu\text{m}) \right)}$$

$$\Rightarrow L = 1.3 \cdot 10^{-7} \frac{(2244 \mu\text{m})^{5/3}}{\left( \frac{2244 \mu\text{m}}{12} + 4 \mu\text{m} + (3-1)(4 \mu\text{m} + 0.5 \mu\text{m}) \right)^{0.083} (4 \mu\text{m} + 0.5 \mu\text{m})^{0.25}}$$

$$\Rightarrow L = 1.3 \cdot 10^{-7} \frac{(2244 \mu\text{m})^{5/3}}{(18.7 \mu\text{m} + 13 \mu\text{m}) (4 \mu\text{m})^{0.083} (4.5 \mu\text{m})^{0.25}}$$

$$\Rightarrow L = 1.3 \cdot 10^{-7} \frac{2244 \mu\text{m}}{143.47 \mu\text{m}} = (1.3 \cdot 10^{-7}) 0.1188 \mu\text{m}$$

$$= 1.53 \cdot 10^{-8} \text{ H}$$

Increase  $N = 4$  will give the  $L$ , closest to the simulation ( $41 \text{nH}$ ).

$$N = 4$$

$$\Rightarrow l_{\text{total}} = 2920 \mu\text{m}.$$

$$L = 1.3 \cdot 10^{-7} \cdot \frac{(2920 \mu\text{m})^{\frac{5}{3}}}{200 \cdot (4)^{0.083} \cdot (4.5)^{0.25} (\mu\text{m})}.$$

$$\Rightarrow L = (1.3 \cdot 10^{-7}) \left( \frac{5.66 \cdot 10^{-5}}{327 \cdot 10^{-6}} \right)$$

$$\Rightarrow L = 2.4 \cdot 10^{-8}$$

$\Rightarrow$  with  $n = 4$ , the result of  $L_1$  is very closed to the simulation.  
 $(2.4 \cdot 10^{-8} \sim 4.1 \cdot 10^{-8})$

Since using the same width, spacing, and metal layers,  
assuming  $L_1 = L_B = 2.4 \cdot 10^{-8}$  with  $N = 4$

$$\Rightarrow L = 2.4 \cdot 10^{-8} \text{ H}$$

### FOR CAPACITOR:

oxide thickness of 200nm and dielectric constant 3.9

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

For the capacitor:

$$100\mu m \times 100\mu m =$$

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$\Rightarrow C = \frac{(8.854 \cdot 10^{-12})(3.9)(100\mu m)^2}{200(10^{-9})}$$

$$\Rightarrow C = 1.72 \cdot 10^{-12} - 17.2 \cdot 10^{-13} \approx 17.2 fF \Rightarrow C_3$$

For the current  $I_{ref}$ :

$$I_{ref} = R = V_{dd} - V_{gs\text{ bias}}$$

$$= 1.5 - 0.814709$$

$$= 0.685 = R$$

$$C = 17.2 fF$$

#### FOR BOND-WIRE PADS:

100um x 100um squares placed at 200um pitch (center to center)

#### FOR THE DIE SIZE:

allow a minimum of 2mm long bond wire;

#### FOR $I_{ref}$ current using resistor instead:

$$I_{ref} = R = 0.685$$

( $V_{dd} - V_{gs}$  of bias transistor).

#### FOR DECOUPLING CAPACITOR:

1-3pF capacitor is used for decoupling of bias line;

$$C_b = 1 pF$$

Schematic:

Hand-drawn LNA Design.

